

UNIT-3
Impedance matching: (P/A) (19)

Quarter Wave Line & Impedance matching: (P/A)

The expression for the input impedance of a dissipationless line may be rearranged as:

$$Z_S = R_0 \left[\frac{Z_R + j R_0 \tan \frac{2\beta S}{2}}{R_0 + j Z_R \tan \frac{2\beta S}{2}} \right]$$

$$= R_0 \tan \frac{2\beta S}{2} \left[\frac{Z_R}{\tan \frac{2\beta S}{2}} + j R_0 \right]$$

$$\frac{\tan \frac{2\beta S}{2} \left[\frac{R_0}{\tan \frac{2\beta S}{2}} + j Z_R \right]}$$

In Quarter wave line $S = \lambda/4$

$$Z_S = R_0 \left[\frac{Z_R}{\tan \frac{2\beta S}{2}} + j R_0 \right]$$

$$\frac{R_0}{\tan \frac{\beta S}{2}} + j Z_R$$

$$= R_0 \times \frac{j R_0}{j Z_R}$$


$$Z_S = \frac{R_0^2}{Z_R}$$

The i/p impedance of one line is equal to the square of R_0 of the line divided by the load impedance.

Application of Quarter wave section:


(1) A quarter wave section of line may be considered as a transformer, to match a load of Z_R to a source of Z_S .

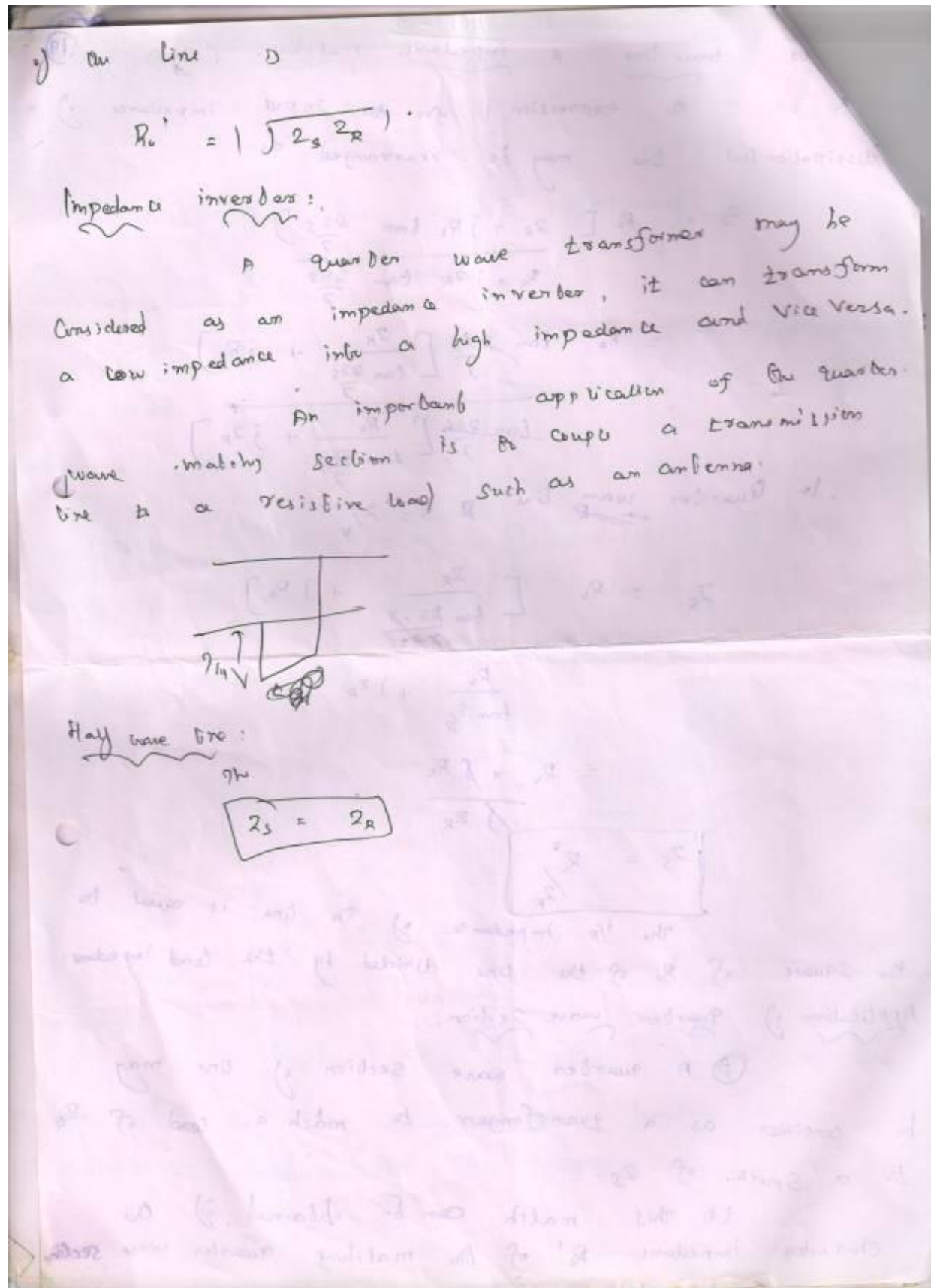(2) This match can be obtained, if the characteristic impedance R_0' of the matching quarter wave section



A quarter wave section of line may be considered as a transformer to match a load of Z_L to source of Z_S .

$$R_0' = \sqrt{Z_S Z_L}$$

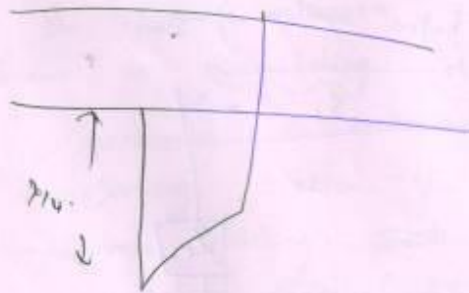

Half wave line:

The input impedance of a dissipation less transmission line is:

$$Z_S = \left[\frac{Z_L + j R_0 \tan \beta l}{R_0 + j Z_L \tan \beta l} \right]$$

For half wave line $l = \lambda/2$.

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$$


$$Z_S = R_0 \left(\frac{Z_L + j R_0 \tan \pi}{R_0 + j Z_L \tan \pi} \right)$$

$$Z_S = R_0 \left(\frac{Z_L}{R_0} \right)$$

$(Z_S = Z_L)$

A quarter wave section of line may be considered as a transformer to match a load of Z_L to source of Z_S .

$$R_0' = \sqrt{Z_S Z_L}$$

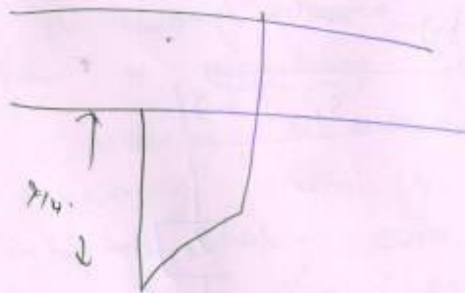

Half wave line:

The input impedance of a dissipation less transmission line is:

$$Z_S = \left[\frac{R_L + j R_0 \tan \beta l}{R_0 + j Z_L \tan \beta l} \right]$$

For half wave line $l = \lambda/2$.

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$$

$$Z_S = R_0 \left(\frac{Z_L + j R_0 \tan \pi}{R_0 + j Z_L \tan \pi} \right)$$

$$\left(Z_S = Z_L \right) = R_0 \left(\frac{Z_L}{R_0} \right)$$

Stub matching :

Single stub matching Double stub matching :

Single stub matching :

min before insertion of stub.

Z_0 Z_R s_1 s_2 d L γ_s γ_0

The input impedance at any point of a transmission line is given by

$$Z_s = Z_0 \frac{Z_R + Z_0 \tanh \gamma l}{Z_0 + Z_R \tanh \gamma l}$$

$$\gamma_s = \gamma_0 \frac{\gamma_R + \gamma_0 \tanh \gamma l}{\gamma_0 + \gamma_R \tanh \gamma l}$$

For propagation $\gamma = j\beta$ ($\alpha = 0$)

$$\gamma_s = \gamma_0 \frac{\gamma_R + j \gamma_0 \tan \beta l}{\gamma_0 + j \gamma_R \tan \beta l}$$

Stub Matching

In general, the source (or) i/p impedance is a fixed one. By selecting the value of load impedance to be equal to the input impedance, impedance matching is achieved.


→ In some cases (load is an antenna), the load impedance is also fixed.
 → If the load impedance is not equal to the input impedance, the maximum power transfer will not take place. This is known as mismatching.

→ So, it is necessary to introduce some form of an impedance transforming section b/w the source & load to achieve impedance matching. Such this section is called an impedance matching device. (eg: quarter wave transformer).

→ Another means of achieve impedance matching is the use of an open (or) short circuited line of suitable length, called stub. This is called stub matching.


There are two types of stub matching.

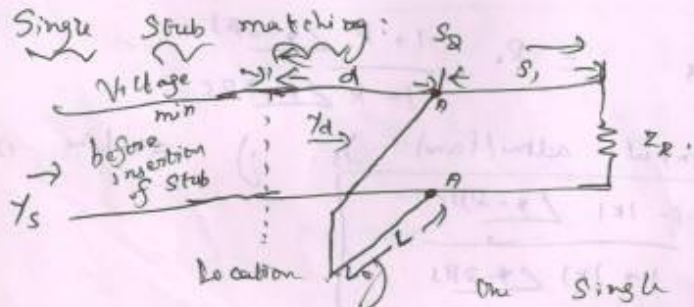- 1. Single stub matching
- 2. Double " "



On single stub for impedance matching the input impedance of the transmission line at point A,

$$Z_s = R_0$$

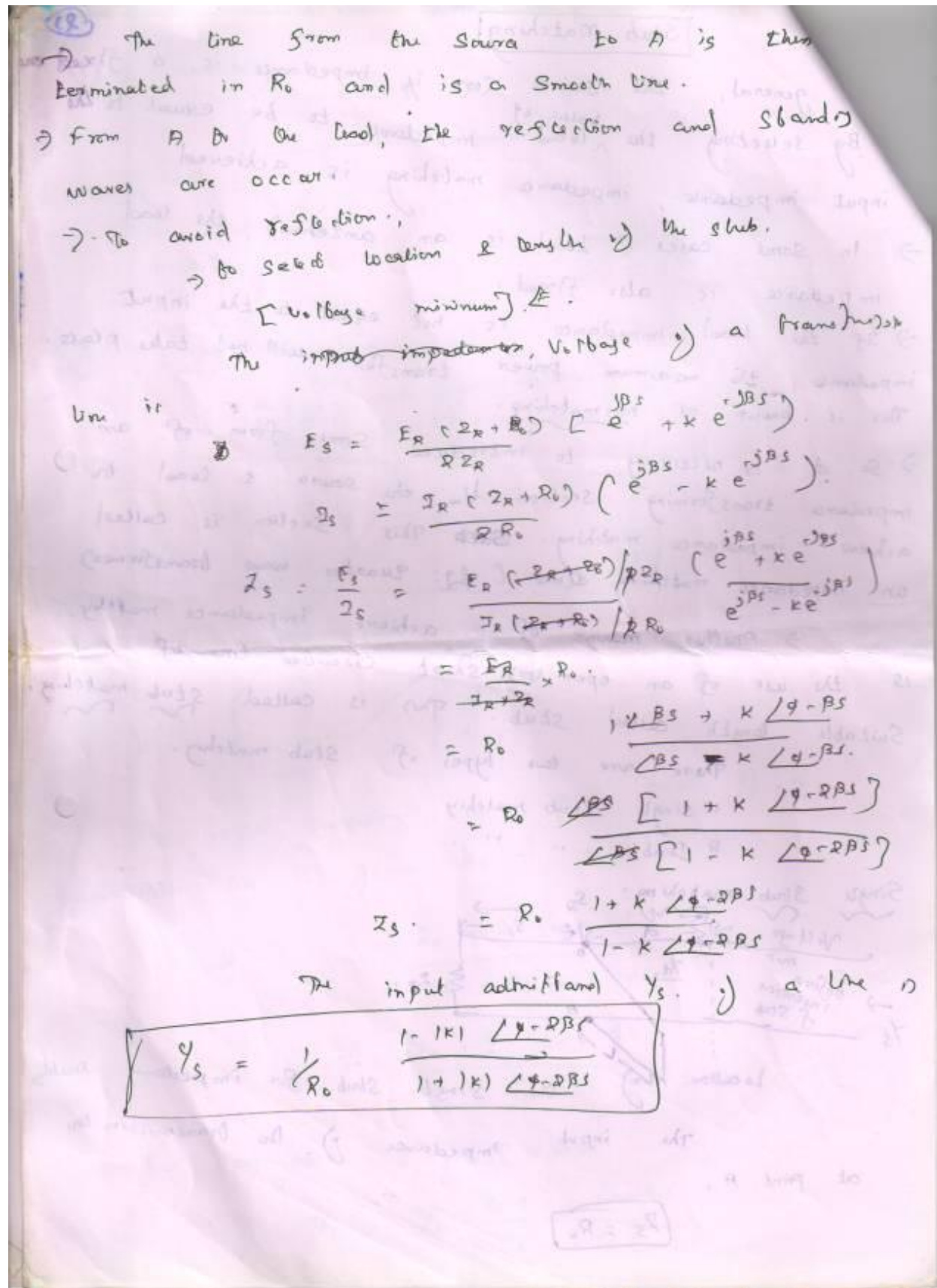

(PS)

$$G_0 = \frac{1}{R_0}$$

$$Y_S = G_0 \left[\frac{1 - |K| \cos(\phi - 2\beta S) - j |K| \sin(\phi - 2\beta S)}{1 + |K| \cos(\phi - 2\beta S) + j |K| \sin(\phi - 2\beta S)} \right]$$

$$= G_0 \left[\frac{1 - |K| \cos(\phi - 2\beta S) - j |K| \sin(\phi - 2\beta S)}{1 + |K| \cos(\phi - 2\beta S) + j |K| \sin(\phi - 2\beta S)} \right]$$

multiply num & denom by $1 - |K| \cos(\phi - 2\beta S) - j |K| \sin(\phi - 2\beta S)$

$$Y_S = G_0 \left[\frac{1 - |K|^2 \cos^2(\phi - 2\beta S) - |K|^2 \sin^2(\phi - 2\beta S) - j |K| \cos(\phi - 2\beta S) + j |K| \cos(\phi - 2\beta S) + |K|^2 \cos^2(\phi - 2\beta S) - j |K| \sin(\phi - 2\beta S) + j |K| \sin(\phi - 2\beta S) + |K|^2 \sin^2(\phi - 2\beta S)}{1 + |K|^2 + 2|K| \cos(\phi - 2\beta S)} \right]$$

$$Y_S = G_0 \left[\frac{1 - |K|^2 - 2j |K| \sin(\phi - 2\beta S)}{1 + |K|^2 + 2|K| \cos(\phi - 2\beta S)} \right]$$

$Y_S = G_S + j B_S$
 Conductance Susceptance

$Y = G + j B$
 $Y = R_{eq}^{-1} + j B_{eq}$

$$\frac{G_S}{G_0} = \frac{1 - |K|^2}{1 + |K|^2 + 2|K| \cos(\phi - 2\beta S)}$$

$$\frac{B_S}{G_0} = \frac{-2|K| \sin(\phi - 2\beta S)}{1 + |K|^2 + 2|K| \cos(\phi - 2\beta S)}$$

Maximum occurs for the value of S at which the cosine term is -1

$$\phi - 2\beta S_2 = -\pi$$


$$2\beta S_2 = \phi + \pi$$


$$S_2 = \frac{\phi + \pi}{2\beta}$$


$$\frac{18}{2+1} = \frac{18}{3} = 6$$


$$\frac{18}{3} = 6$$

$$\frac{18}{1} = 18$$

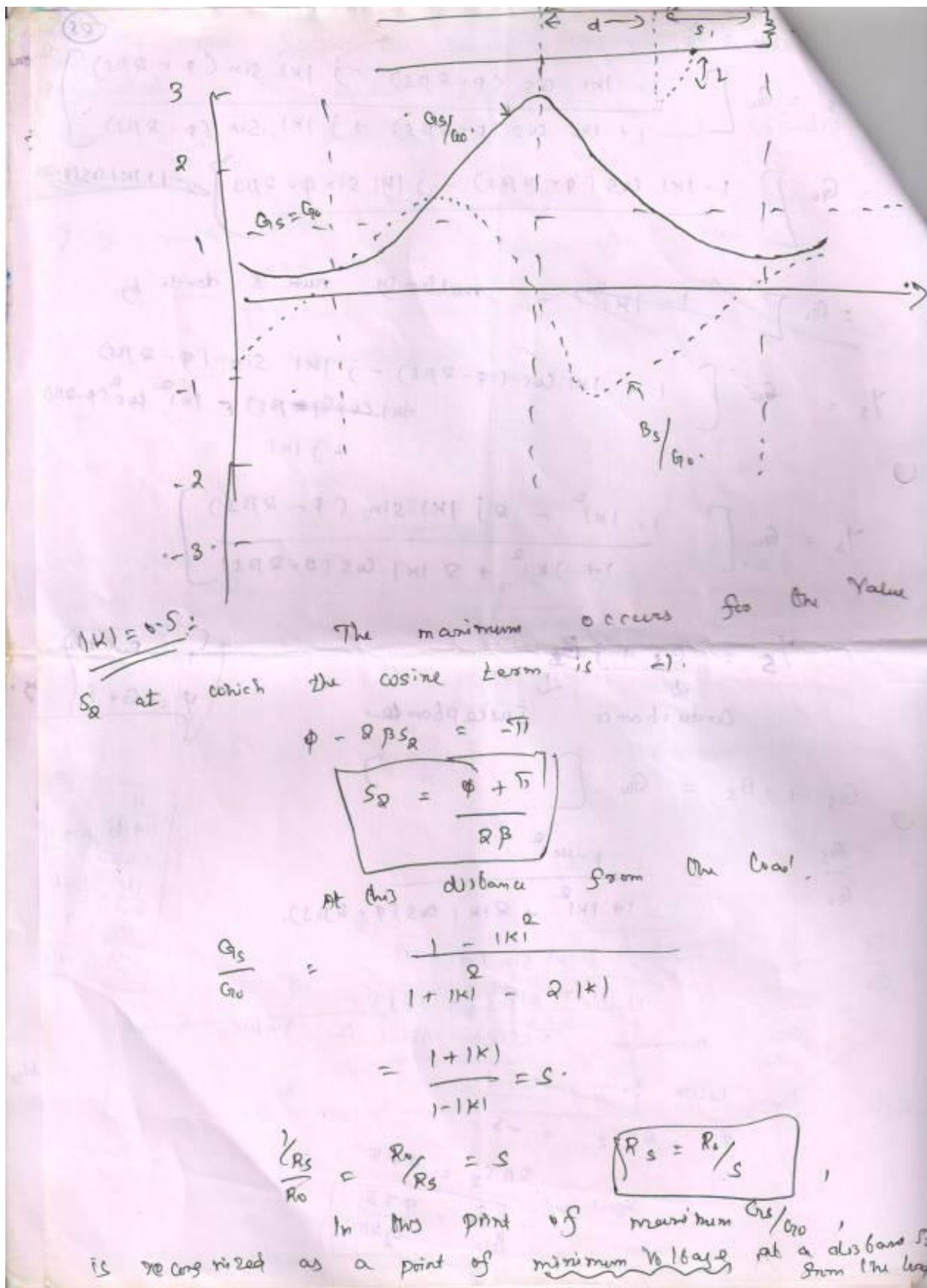

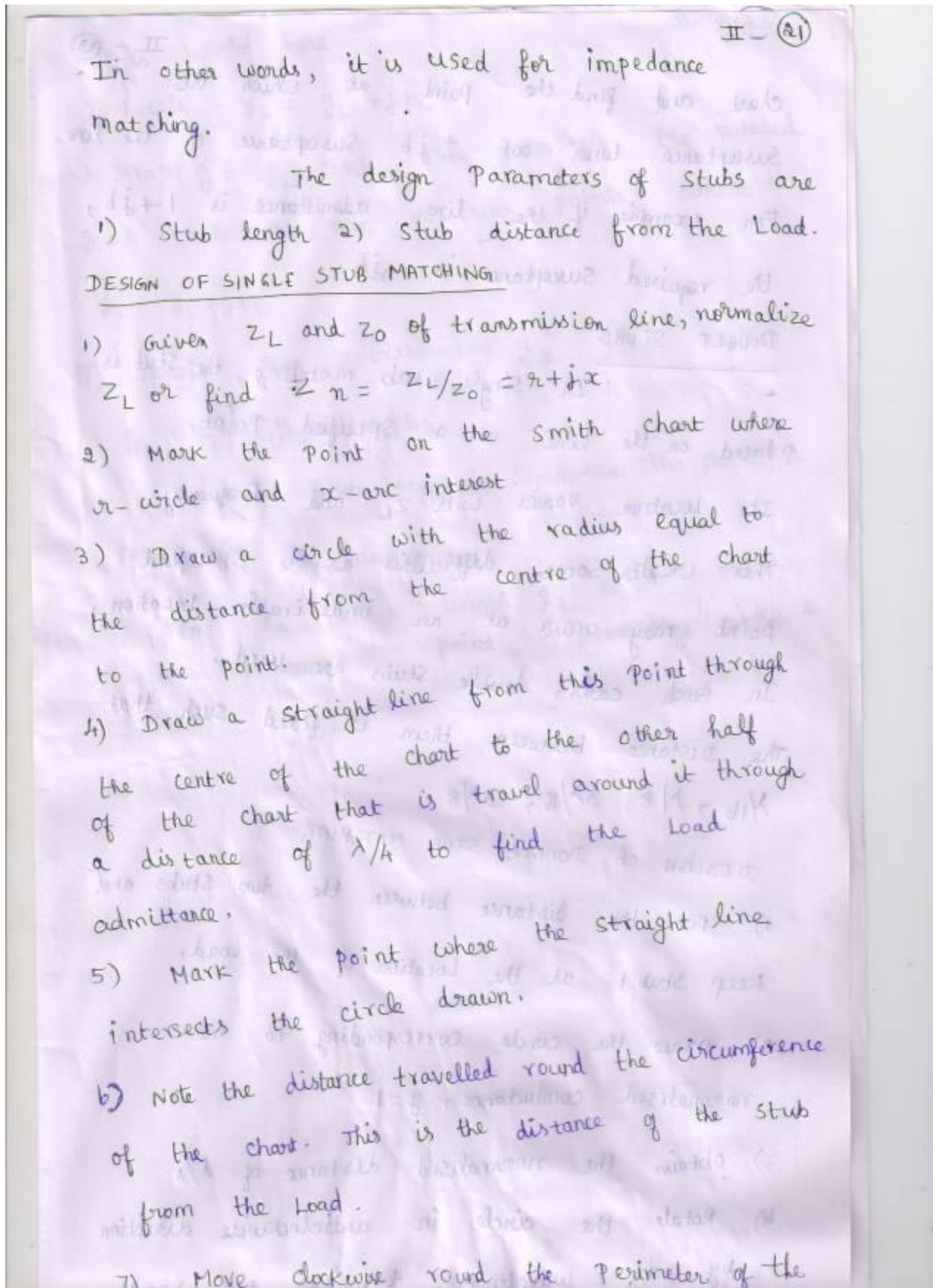

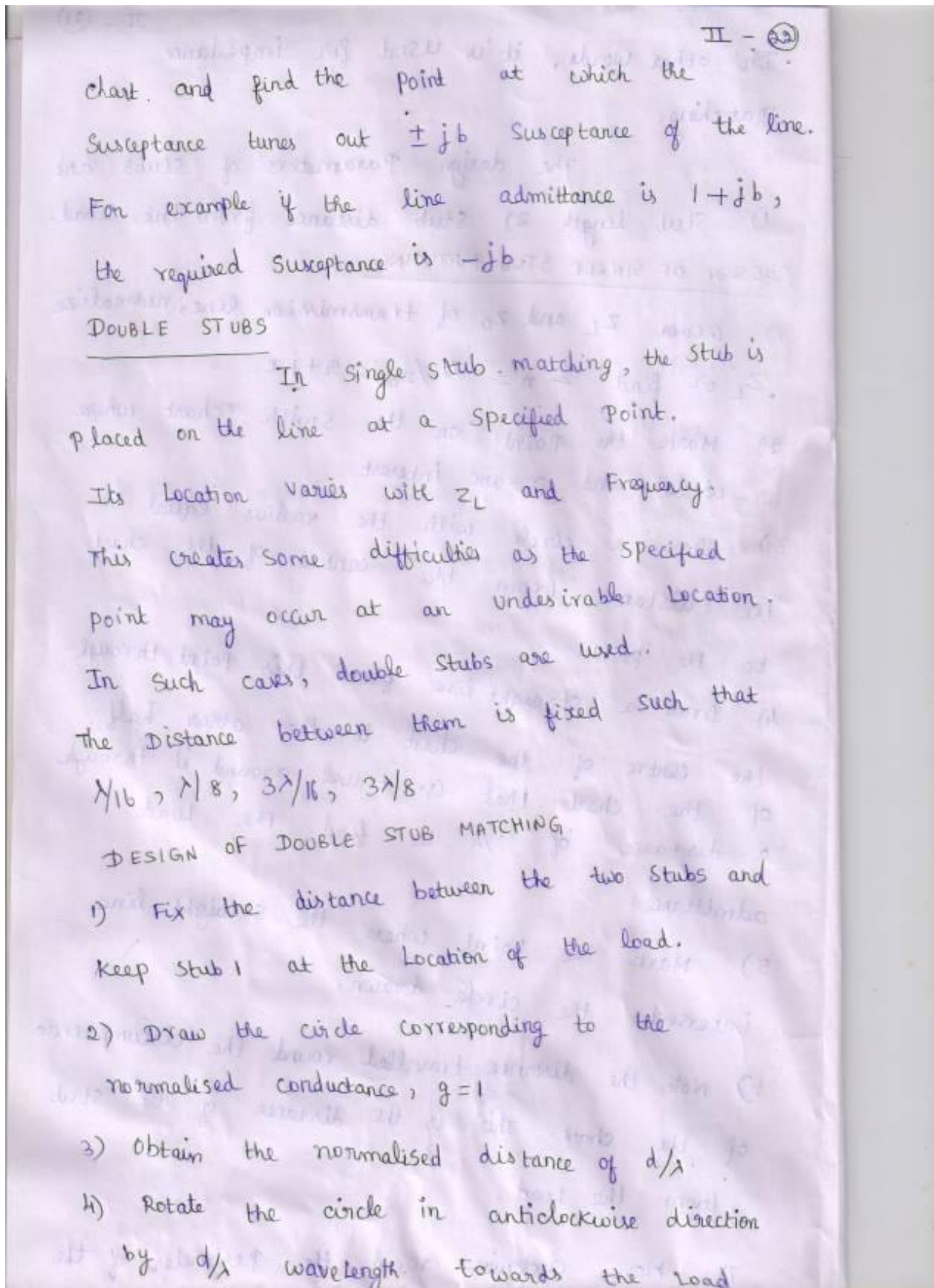

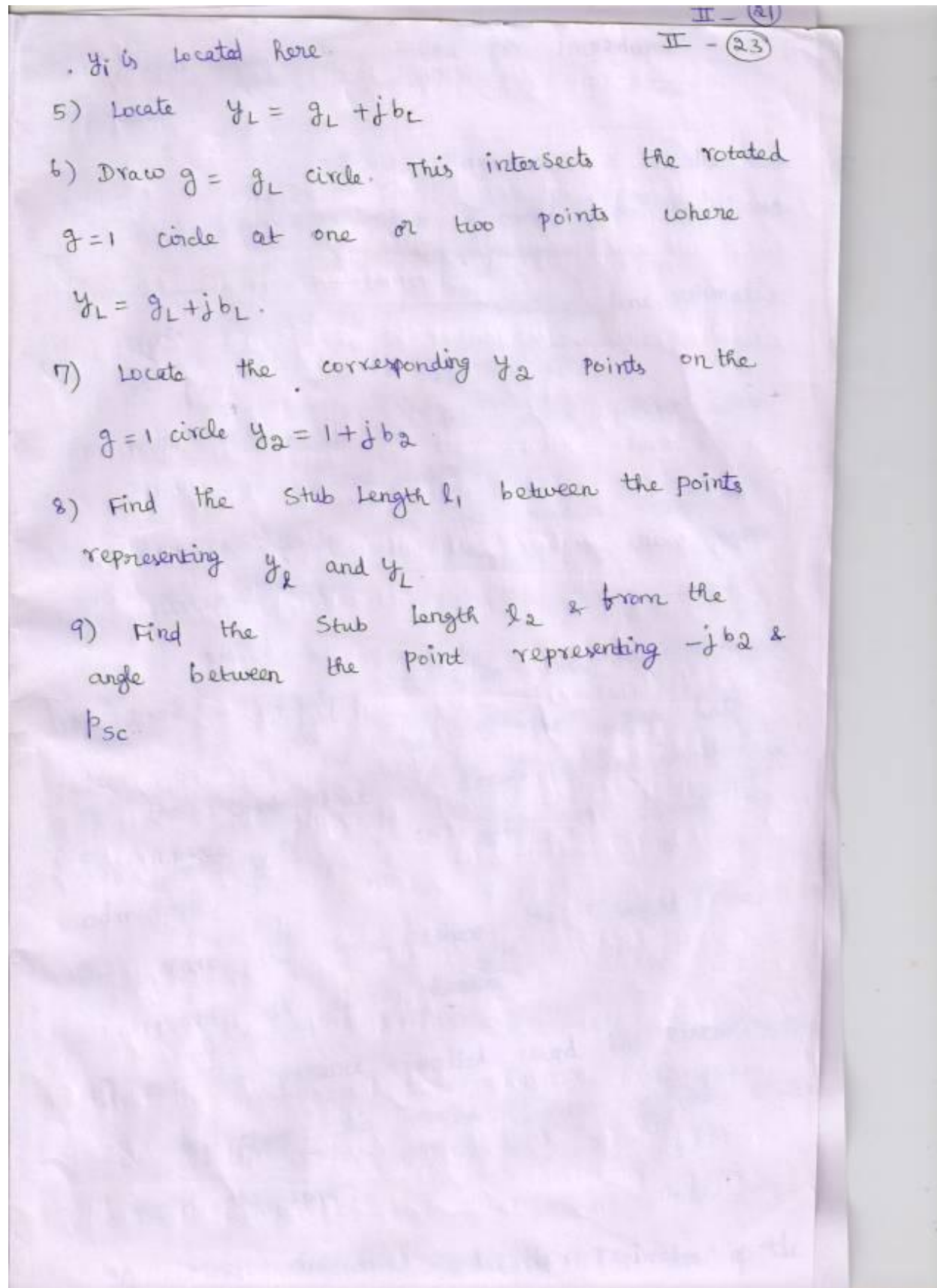

46

Input Impedance of a dissipationless line at any point distance S away from load is $Z_S = Z_0 \left[\frac{Z_R + j Z_0 \tan \beta S}{Z_0 + j Z_R \tan \beta S} \right]$

$$Y_S = \frac{Y_R + j \tan \beta S}{1 + j Y_R \tan \beta S}$$

$$Y_S = \frac{Y_R (1 + \tan^2 \beta S)}{1 + Y_R^2 \tan^2 \beta S} + j \frac{(1 - Y_R^2) \tan \beta S}{1 + Y_R^2 \tan^2 \beta S}$$


Two stubs are separated by fixed distances $\frac{\lambda}{16}, \frac{\lambda}{8}, \frac{3\lambda}{16}, \frac{3\lambda}{8}$ etc....

CIRCLE DIAGRAM, SMITH CHART AND ITS APPLICATIONS:

SMITH CHART - THE SMITH CIRCLE DIAGRAM:

The Smith chart is a valuable Graphical tool for solving radio frequency transmission line problems.

SMITH CHART CIRCLE DIAGRAMS:

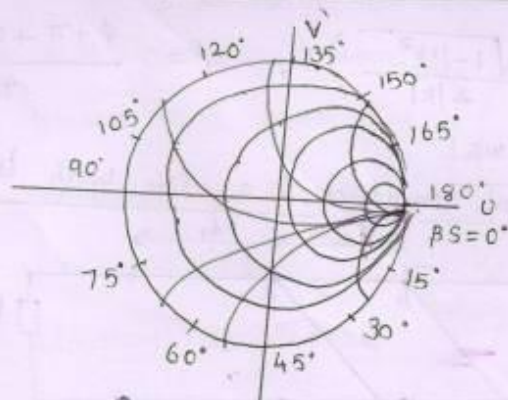

APPLICATIONS OF THE SMITH CHART:

1. Plotting an Impedance
2. Measurement of VSWR
3. Measurement of Reflection Coefficient K [magnitude and phase]
4. Measurement of Input Impedance of the line.
5. Measurement of Impedance to Admittance Conversion.

1. Plotting an Impedance:

$$\text{Normalized Impedance } z_R = \frac{Z_R}{R_0} = \frac{60 + j40}{50} = 1.2 + j0.8$$

The intersection of the two circles is represented by the dotted lines and the point P indicates the normalized impedance on the chart.

2. Measurement of VSWR:

Point of intersection of S-circle with the real axis at the right side of the centre indicates a VSWR for given line. - Select a centre of the circle as point $O(1,0)$, Take a distance from O to the point P indicating normalized impedance and then draw a circle. The circle cuts the horizontal real axis. This indicates the value of VSWR.

3. Measurement of Reflection Coefficient K [magnitude and phase]:

The angle of the reflection coefficient K can be obtained by extending a line from center to the

outer rim of the chart through the point which indicates the normalized impedance. The point at which the extended line cuts the outer rim gives directly the value of angle of the reflection coefficient K .

4. Measurement of input impedance of the line:

Calculate length in terms of λ or degrees.

$$\lambda = \frac{v}{f} = \frac{0.6c}{f} = \frac{0.6 \times 3 \times 10^8}{2 \times 10^6} = 90 \text{ m.}$$

$$S = 30 \text{ m} = \frac{30}{90} \lambda = \frac{\lambda}{3} \text{ m or } \frac{720}{3} = 240^\circ$$

Normalized input impedance represented by point T is.

$$Z_{in} = 0.48 + j0.035$$

The actual value of the input impedance is.

$$Z_{in} = R_0 (Z_{in}) = 50 (0.48 + j0.035) = 24 + j1.75 \Omega$$

5. Impedance to Admittance Conversion:

The terminating impedance is.

$$Z_R = 60 + j40$$

Terminating admittance is

$$Y_R = \frac{1}{Z_R} = \frac{1}{60 + j40} = \frac{1}{72.111 \angle 33.69^\circ} = 0.01386 \angle -$$

$$= 0.0115 - j7.688 \times 10^{-3} \text{ S}$$

$$Y_R = 0.58 - j0.4$$

The actual value of the admittance is

$$G_0 [Y_R] = \frac{1}{R_0} [Y_R] = \frac{0.58 - j0.4}{50} = 0.0116 - j0.008$$

(49)

Problem Solving Using Smith chart:

① An R.F. Transmission line with a characteristic impedance of $300 \angle 0^\circ \Omega$ is terminated in an impedance of $100 \angle -45^\circ \Omega$. The load is to be matched to the transmission line by using a short circuited stub. With the help of Smith chart. Determine the length of the stub and the distance from the load.

Solution:

$$Z_R = 100 \angle -45^\circ \Omega = (70.71 - j70.71) \Omega$$

$$Z_0 = R_0 = 300 \angle 0^\circ = 300 \Omega$$

- The normalized impedance is

$$z_R = \frac{Z_R}{Z_0} = \frac{Z_R}{Z_0} = \frac{70.71 - j70.71}{300} = 0.2357 - j0.2357$$
- Locate point A, the intersection of $r = 0.2357$ circle and $x = -0.2357$ circle. As the imaginary component (ie) reactive component of the impedance is negative, the point A is located below the horizontal axis.
- Draw a circle with O as origin and OA as radius. This is constant S-circle. It cuts real axis. This is the value of S before stub connection.
- Draw line from point A to O and extend to reach other end on constant S circle. In the chart A, this point is represented as B at which the normalized admittance is $Y_R = 2.1 + j2.1$. Extend line AOB to the outer rim upto point B.
- Travel along the constant S-circle in the clockwise direction from load to generator to reach a point