

UNIT-III ASYNCHRONOUS SEQUENTIAL CIRCUITS**TWO MARKS****1. What are secondary variables?**

-present state variables in asynchronous sequential circuits

2. What are excitation variables?

-next state variables in asynchronous sequential circuits

3. What is fundamental mode sequential circuit?

-input variables changes if the circuit is stable

-inputs are levels, not pulses

-only one input can change at a given time

-input variables changes if the circuit is stable

-inputs are levels, not pulses

-only one input can change at a given time

4. What is pulse mode circuit?

-inputs are pulses

-widths of pulses are long for circuit to respond to the input

-pulse width must not be so long that it is still present after the new state is reached

5. What are the significance of state assignment?

∞ In synchronous circuits-state assignments are made with the objective of circuit

reduction

∞ Asynchronous circuits-its objective is to avoid critical races

6. When does race condition occur?

-Two or more binary state variables change their value in response to the change in i/p Variable

7. What is non critical race?

Final stable state does not depend on the order in which the state variable changes race condition is not harmful

8. What is critical race?

-final stable state depends on the order in which the state variable changes -race condition is harmful

9. When does a cycle occur?

-asynchronous circuit makes a transition through a series of unstable state

10. What are the different techniques used in state assignment?

-shared row state assignment

-One hot state assignment

11. What are the steps for the design of asynchronous sequential circuit?

-construction of primitive flow table -reduction of flow table

-state assignment is made -realization of primitive flow table

12. What is hazard?

-unwanted switching transients

13. What is static 1 hazard?

-output goes momentarily 0 when it should remain at 1

14. What are static 0 hazards?

-output goes momentarily 1 when it should remain at 0

15. What is dynamic hazard?

-output changes 3 or more times when it changes from 1 to 0 or 0 to 1

16. What is the cause for essential hazards?

-unequal delays along 2 or more path from same input

17. What is flow table?

-state table of an synchronous sequential network

18. What is SM chart?

-describes the behavior of a state machine

-used in hardware design of digital systems

19. What are the advantages of SM chart?

-easy to understand the operation

-easy to convert to several equivalent forms

20. What is primitive flow chart?

-one stable state per row

21. What is state equivalence theorem?

Two states SA and SB, are equivalent if and only if for every possible input X sequence, the outputs are the same and the next states are equivalent i.e., if $SA(t+1) = SB(t+1)$ and $ZA = ZB$ then $SA = SB$.

22. What do you mean by distinguishing sequences?

Two states, SA and SB of sequential machine are distinguishable if and only if there exists at least one finite input sequence. Which, when applied to sequential machine causes different output sequences depending on whether SA or SB is the initial state.

23. Prove that the equivalence partition is unique

Consider that there are two equivalence partitions exist: PA and PB, and PA) PB. This states that, there exist 2 states Si & Sj which are in the same block of one partition and not in the same block of the other. If Si & Sj are in different blocks of say PB, there exists at least one input sequence which distinguishes Si & Sj and therefore, they cannot be in the same block of PA.

24. Define compatibility.

States Si and Sj said to be compatible states, if and only if for every input sequence that affects the two states, the same output sequence, occurs whenever both outputs are specified and regardless of whether Si or Sj is the initial state.

25. Define merger graph.

The merger graph is defined as follows. It contains the same number of vertices as the state table contains states. A line drawn between the two state vertices indicates each compatible state pair. If two states are incompatible no connecting line is drawn.

26. Define incompatibility

The states are said to be incompatible if no line is drawn in between them. If implied states are incompatible, they are crossed & the corresponding line is ignored

27. Explain the procedure for state minimization.

1. Partition the states into subsets such that all states in the same subsets are 1 - equivalent.

2. Partition the states into subsets such that all states in the same subsets are 2 - equivalent.

3. Partition the states into subsets such that all states in the same subsets are 3 -

equivalent.

28. Define closed covering.

A Set of compatibles is said to be closed if, for every compatible contained in the set, all its implied compatibles are also contained in the set. A closed set of compatibles, which contains all the states of M, is called a closed covering.

29. Define machine equivalence.

Two machines, M1 and M2 are said to be equivalent if and only if, for every state in M1, there is a corresponding equivalent state in M2 & vice versa.

30. Define state table.

For the design of sequential counters we have to relate present states and next states. The table, which represents the relationship between present states and next states, is called state table.

31. Define total state.

The combination of level signals that appear at the inputs and the outputs of the delays define what is called the total state of the circuit.

32. What are the steps for the design of asynchronous sequential circuit?

1. Construction of a primitive flow table from the problem statement.
2. Primitive flow table is reduced by eliminating redundant states using the state Reduction
3. State assignment is made
4. The primitive flow table is realized using appropriate logic elements.

33. Define primitive flow table.

It is defined as a flow table which has exactly one stable state for each row in the table. The design process begins with the construction of primitive flow table.

34. What are the types of asynchronous circuits?

1. Fundamental mode circuits
2. Pulse mode circuits

35. Give the comparison between state Assignment Synchronous circuit and state assignment asynchronous circuit.

In synchronous circuit, the state assignments are made with the objective of circuit reduction. In asynchronous circuits, the objective of state assignment is to avoid critical races.

36. What are races?

When 2 or more binary state variables change their value in response to a change in an input variable, race condition occurs in an asynchronous sequential circuit. In case of unequal delays, a race condition may cause the state variables to change in an unpredictable manner.

37. Define non critical race.

If the final stable state that the circuit reaches does not depend on the order in which the state variable changes, the race condition is not harmful and it is called a non critical race.

38. Define critical race?

If the final stable state depends on the order in which the state variable changes, the race condition is harmful and it is called a critical race.

39. What is a cycle?

A cycle occurs when an asynchronous circuit makes a transition through a series of unstable states. If a cycle does not contain a stable state, the circuit will go from one unstable to stable to another, until the inputs are changed.

40. List the different techniques used for state assignment.

1. Shared row state assignment
2. One hot state assignment.

41. Write a short note on fundamental mode asynchronous circuit.

Fundamental mode circuit assumes that. The input variables change only when the circuit is stable. Only one input variable can change at a given time and inputs are levels and not pulses.

42. Write a short note on pulse mode circuit.

Pulse mode circuit assumes that the input variables are pulses instead of level. The width of the pulses is long enough for the circuit to respond to the input and the pulse width must not be so long that it is still present after the new state is reached.

43. Write short note on shared row state assignment.

Races can be avoided by making a proper binary assignment to the state variables. Here, the state variables are assigned with binary numbers in such a way that only one state variable can change at any one state variable can change at any one time when a state transition occurs. To accomplish this, it is necessary that states between which transitions occur be given adjacent assignments. Two binary are said to be adjacent if they differ in only one variable.

44. Write short note on one hot state assignment.

The one hot state assignment is another method for finding a race free state assignment. In this method, only one variable is active or hot for each row in the original flow table, ie, it requires one state variable for each row of the flow table. Additional row are introduced to provide single variable changes between internal state transitions.

PART B

A sequential circuit has 2D ff's A and B an input x and output y is specified by the following next state and output equations.

- a. $A(t+1) = Ax + Bx$
- b. $B(t+1) = A'x$
- c. $Y = (A+B)x'$

- (i) Draw the logic diagram of the circuit.
- (ii) Derive the state table.

(iii) Derive the state diagram.

2. Design a mod-10 synchronous counter using Jk ff. write excitation table and state

table.

3. a) Write the excitation tables of SR, JK, D, and T Flip flops (b) Realize D and T flip flops using Jk flip flops
4. Design a sequential circuit using JK flip-flop for the following state table [use state

diagram]

Present state AB	Next state		Output	
	X=0	X=1	X=0	X=1
00	00	11	1	0
01	01	11	1	1
10	01	00	1	0
11	11	10	0	0

5. Design a counter with the following repeated binary sequence:0, 1, 2, 3, 4, 5, 6.use JK Flip-flop.
6. Design a 3 bit synchronous gray code counter using flip flop.
7. Draw and explain the block diagram of Mealy circuit.
8. Using positive edge triggering SR flip-flops design a counter which counts in the following sequence: 000,111,110,101,100,011,010,001,000,...