

## UNIT-II - TRANSISTORS


1. Calculate  $\beta$  of a transistor when  $\beta_{DC} = 0.98$

$$\beta = \beta_{DC} / (1 - \beta_{DC}) = 0.98 / (1 - 0.98) = 49$$

2. Among CE, CB and CC configurations, which one is the popular? Why?

→ The CE configuration is widely used because it provides both voltage gain as well as current gain greater than unity.

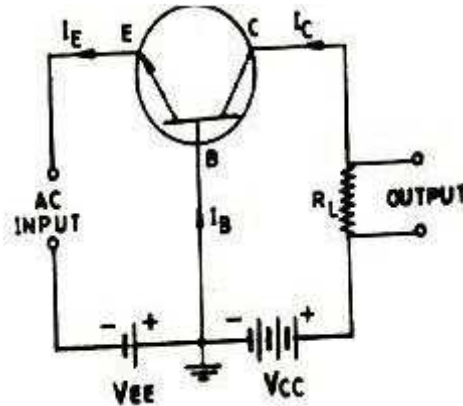3. Draw the circuit of NPN transistor in CB configuration?



4. What are power transistors? List its applications.

→ Power transistors are designed for power amplification which means that the operating voltage and current must be large.

### Applications:

1. They are used in switching power supplies.
2. They are used in audio power amplifiers.

5. What is the relation between  $I_B$ ,  $I_E$  and  $I_C$  in CB configuration?

$$\text{Emitter current } I_E = I_B + I_C$$

6. Name the operating modes of a transistor?

1. Cut off
2. Active
3. Saturation

7. What are hybrid parameters


$$h_{11} = V_i / I_i | V_0 = 0 \quad h_{21} = I_0 / I_i | V_0 = 0$$

$$h_{12} = V_i / V_0 | I_0 = 0 \quad h_{22} = I_0 / V_0 | I_i = 0$$

**8. What is the application of optocoupler?**

The application of optocoupler is to provide electrical isolation between input and output circuit.

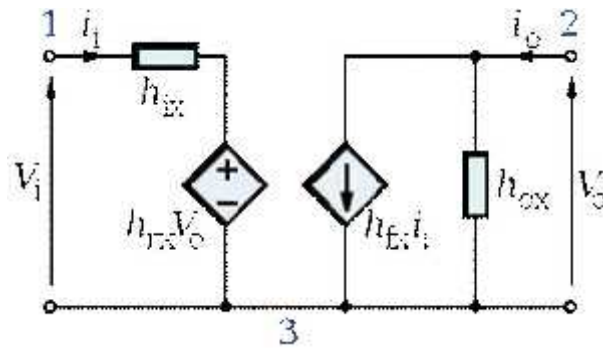**9. Draw the h-parameter equivalent circuit of a CE BJT configuration?**



**10. Give the  $h_{ie}$  and  $h_{oe}$  equations of BJT**

$$h_{ie} = \left. \frac{V_{BE}}{I_B} \right|_{V_{CE} \text{ Constant}}$$

$$h_{oe} = \left. \frac{I_C}{V_{CE}} \right|_{I_B \text{ Constant}}$$

**11. When does a transistor acts as a switch?**

The transistor acts as a switch when it is operated at either cutoff region or saturation region.

UNIT-II

TRANSISTORS.

1. Comparison of D-MOSFET & E-MOSFET. (8)

S.No.	Enhancement MOSFET	Depletion MOSFET.
1.	Gate - +ve	Gate - -ve.
2.	Channel - Not diffused	Channel - diffused
3.	Drain current ↑ with ↑ in gate V <sub>gs</sub> .	Drain current ↓ with ↓ in -ve gate voltage.
4.	Both P-N channel exist	Both P-N channel exist
5.	E-type can't be used as D-type	D-type can be used as E-type
6.	I <sub>D</sub> → negligible, V <sub>GS</sub> = 0	I <sub>D</sub> - Consider at V <sub>GS</sub> = 0.
7.	Useful in switching application	less preferred.

2) Compare the following N-channel & P-channel MOSFET (8)

S.No	N-channel MOSFET	P-channel MOSFET.
1.	ON substance - small, occupies less space.	ON resistance - high.
2.	Size small, C <sub>T</sub> - small.	mobility of electrons is 2 1/2 of holes
3.	+ve gate drain supply	Size → greater, C <sub>T</sub> reduces speed
4.	cooler.	-ve gate drain.
5.	Saturation region (V <sub>DS</sub> > V <sub>DS(sat)</sub> )	Cheaper.
6.	Non " " (V <sub>DS</sub> < V <sub>DS(sat)</sub> )	Saturation region V <sub>SD</sub> > V <sub>SD(sat)</sub>
7.	Transition point V <sub>DS</sub> = V <sub>GS</sub> - V <sub>TP</sub>	Non " " V <sub>SD</sub> < V <sub>SD(sat)</sub>
		V <sub>SD</sub> = V <sub>GS</sub> + V <sub>TP</sub> .

3) Explain the biasing technique of JFET. (16)

- \* Necessary to maintain the operating point Q stable in the central portion of the pinch off region. V<sub>GS</sub> & I<sub>D</sub> - biasing
- \* Combination of self bias & fixed bias to provide stability.

8. Explain the working of LCD seven segment display using square wave supply (2).

\* LCD - Liquid Crystal Display are used for display of numeric & alpha-numeric character in dot-matrix and segment displays. (2)

\* Construction - two types. (i) Dynamic scattering type (1)  
(ii) field effect type (1)

\* Working (2) \* Diagram (2)

9. Explain Insulator, Semiconductor & conductor with help of Energy band structure (2) Diagram of Energy bands (2)

Insulator (2): which 8 valence electrons are bound tight to parent atoms

\* eg (paper, mica etc.)

\* Properties  $\rightarrow$  conductivity, melting & boiling temp  $\uparrow$

Conductor (2): Electron at outermost orbit of an atom moves freely.

\* Properties - conductivity, melting & boiling temp  $\downarrow$

\* eg (copper, iron etc.)

Semiconductor (2): 4 valence electrons, b/w insulator & conductor.

\* Properties  $\rightarrow$  conductivity, melting & boiling temp.

\* Eg (Silicon, germanium etc.)

10. Write down the expression for transition capacitance & diffusion capacitance (8)

Transition capacitance (4): \* Reverse bias - majority carrier more  
( $C_T$ ) \* Depletion layer widens.

\*  $C_T = \left| \frac{dq}{dv} \right|$  (i) Alloy junction  
(ii) Grown junction

Diffusion capacitance (4): \*  $C_T = q \cdot N_p \cdot A \left( \frac{\tau}{q N_D W} \right)$ ;  $C_T = \frac{qA}{W}$   
(2)

\* Injected charge storage near the junction.

\*  $C_D = \tau I$ ;  $C_D = \frac{\tau I}{V_T}$  \* for reverse bias,  $C_D$  - neglected  
\* for forward bias,  $C_D > C_T$

\* Self bias diagram (1)  $V_{DD}$  applied,  $I_D$  flows in absence of  $V_G$ .

$$V_S = I_D R_S \quad V_D = V_{DD} - I_D R_D$$

Drain to source voltage:  $V_{DS} = V_{DD} - I_D (R_D + R_S)$

Gate to source voltage:  $V_{GS} = -I_D R_S$

$I_D \uparrow$ , voltage drop  $\uparrow$ .  $\uparrow V_{GS}$ ,  $\downarrow$  width of channel,  $\rightarrow \downarrow I_D$

$I_D \downarrow \rightarrow V_{GS} \downarrow$ ,  $\uparrow$  width of channel  $\uparrow I_D$ .

\* Voltage divider bias:  $V_{GG} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$ ;  $R_g = \frac{R_1 R_2}{R_1 + R_2}$

diagram (1)  $V_{GG} \gg V_{GS}$ .  $I_D \approx$  constant.

$V_{GS}$  can vary several volts from one JFET to another.

f. Explain the construction & characteristics of JFET (16)

Construction (8): FET consists of p-type (or) N-type silicon bar containing two PN junctions at the sides.

Notation: Gate (G), Drain (D), Source (S) channel.

Source & Drain may be interchanged.

Diagram for N-channel FET

$I_S, I_D, I_G \rightarrow$  +ve direction

N-channel:  $V_{DS}$  - +ve,  $V_{GS}$  -ve.

Diagram for p-channel FET

direction of arrow  $\rightarrow$  gate junction

p-channel:  $I_D, V_{DS}$  -ve  
 $V_{GS}$  +ve.

\* when  $V_{GG}$  applied &  $V_D = 0$ . - depletion region.

\* when  $V_{DD}$  applied &  $V_{GG} = 0$

\* when  $V_{DD}$  &  $V_{GG}$  applied. - pinch-off voltage.

Characteristics of JFET (8) Relate the current & voltage

Transfer characteristics (4)

Drain characteristics (4)

$$I_D, V_{GS} \text{ & } V_{DS} \quad I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

Diagram

5. Explain the construction & Characteristics of E-MOSFET (16)

Construction (8) → No depletion mode.

→ Operated with +ve gate to source voltage  $V_{GS}$ .

→  $V_{GS} = 0, V_{DS} \rightarrow$  tries to force electron from source to drain

→ No drain current  $V_{GS} = 0$ .

\* Diagram; → Inversion layer.

→ Minimum gate to source voltage → Threshold Voltage.

\*  $V_{GS} < V_{GS(th)} \rightarrow$  NO current flows from D to S

\*  $V_{GS} > V_{GS(th)} \rightarrow$  Value of current.

Characteristics (8) (i) Drain characteristics (4) (ii) Transfer characteristics (4)

Diagram →  $V_{GS}, V_G, I_D$  curve &  $V_{GS}, V_G, I_{DSS}$  curve.

$I_D \uparrow$  with  $\uparrow$  in  $V_{GS}$ .

$$I_D = k [V_{GS} - V_{GS(th)}]^2 \quad V_{GS} > 0.$$

6. Explain the construction & characteristics of D-MOSFET (16)

Construction (8): operate in two diff. modes → Depletion & Enhancement mode.

Depletion mode (4): -ve gate voltage depletes the channel of free electrons.

Diagram

Enhancement mode (4):  $V_{GS} \rightarrow$  +ve.  $\uparrow$  the no. of free electrons enhance the conduction of channel.

Diagram.

Characteristics (8):

Drain characteristics (4): Above  $V_{GS} = 0$  +ve, below -ve.  
 $\downarrow$  Enhancement mode  $\rightarrow$  depletion mode.

$V_{DS} = 0$ . No conduction.

$V_{GS} > 0$ , gate induce more electrons

Transfer characteristics (4):  $V_{GS}$  extends.  $I_{DSS} \rightarrow$  D to S with  $V_{GS} = 0$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \quad \text{Normally ON mosfet.}$$

$V_{GS} > 0, I_D \uparrow$ .

7. Explain the biasing characteristics of MOSFET. (16)

Biasing the Enhancement MOSFET (8): Drain to gate bias

\* diagram ;  $V_{GS} = \left[ \frac{R_1}{R_1 + R_2} \right] V_{DD}$ . DC stabilisation through  $R_f$ .  
 $V_{GS}$  is reduced.

D.C stability by D.C feedback thro  $R_s$ .

$$V_{GS} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} \quad V_{GS} = V_{DD} - V_G$$

\*  $V_{GS} > V_{TN}$ ,  $I_D = K_N (V_{GS} - V_{TN})^2$ ;  $V_{DS} = V_{DD} - I_D R_D$ .

$V_{DS} > V_{DS}(sat) \rightarrow$  Saturation region

$V_{DS} < V_{DS}(sat) \rightarrow$  Non-saturation  $\therefore I_D = K_N [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$

Biasing of depletion MOSFET (8):

Biasing the self  $\gamma$  voltage bias circuit given for JFET used to establish operating point Diagram

\* Self bias (4):  $V_{GS} = -I_D R_s$ ;  $V_{DS} = V_{DD} - I_D (R_D + R_s)$

\* Voltage divider bias (4):  $V_{GS} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$ .  $V_{GS} = V_{GS} - I_D R_s$ .

8) Explain the working principle of operation of UJT & mention its application (16).

UJT - Uni Junction Transistor  $\rightarrow$  Only one PN junction  
 $\rightarrow$  3 terminal silicon diode  
 $\rightarrow$  Ability to control large AC power with small input IP.  
 $\rightarrow$  -ve resistance char. which use as oscillator.

Principle (2)      Operation (2)  
 Construction (2)      Diagram (2)  
 Working (4)  
 Application (4)  $\rightarrow$  Intrinsic standoff ratio  $\eta = \frac{R_{B1}}{R_{B1} + R_{B2}} = 1$

$\rightarrow$  When no voltage is applied to emitter

$\rightarrow$  When +ve " " " " "

$\rightarrow$  VI - Characteristics of UJT:  $I_E$  Vs  $V_E$ . \* Valley point.  
 Saturation region.

Application: switching ckt, pulse generation, timing trigger ckt.

9. Explain the working and characteristics of SCR and its application (16)

SCR - Silicon Controlled Rectifier. → Four layered PNPN device.

→ Used as switching device.

Construction: Diagram; Anode, Cathode, Gate.

Biasing:  $J_1$  &  $J_2$  → forward bias while  $J_2$  → Reverse bias.

Operation: → load in series with anode, gate open. No Ige.

→ Cutoff state.

→ Anode voltage ↑ to breakover voltage. ON state.

→ OFF state → No current flow through the device.

→ Called as Unidirectional device.

V-I characteristics: → forward:  $I_G = 0$  (forward blocking region  
" conduction ")  
→ Reverse: .

Applications: relay controls, static switches, heater control etc.,

10. Briefly explain the operation of TRIAC & DIAC (16)

TRIAC - Triode A.C switch → Three terminal semiconductor device

(8)

(diagram &

characteristic curve)

→  $MT_1$ ,  $MT_2$  & gate.

→ Equivalent to 2 SCR in parallel but in reverse direction

→ Leakage current - small.

→ Device - starts conducting → high current flow.

→ Bidirectional device.

→ Used for illumination, temperature control.

DIAC (8) - Diode A.C switch. - 3 layers 2 terminal device

→ Not a control device.

→  $MT_1$ ,  $MT_2$ . Bidirectional avalanche diode

→ Identical char for +ve & -ve half of a.c

→ Used as triggering device.

→  $V_{ge} < \text{breakover voltage}$  → current almost.

→ reaches breakover, exhibit -ve resistance

→ current ↑, voltage decreasing.