

## UNIT-V – FEEDBACK AMPLIFIERS AND OSCILLATORS

### **1. What are the types of Multivibrators**

The three types of multivibrators are

1. bistable :It has two stable states.
2. It has one stable state.
3. It has two states both are quasi-stable.

### **2. What is intrinsic standoff ratio of a UJT**

Intrinsic stand-off ratio of UJT indicates that the transistor internally divides the supply voltage and bias the emitter terminal. It is the ratio of the stand off voltage to the power supply voltage.

### **3. What is a clamper? Name its types?**

The circuit which is used to add a d.c level as per the requirements to the a.c output signal is called Clamper circuit. The two types are positive clamper and negative clamper.

### **4. How is a Schmitt trigger different from a multivibrator?**

A Schmitt trigger is a threshold circuit which uses positive feedback with loop gain greater than unity. The Schmitt trigger is a comparator which switches the output positive when the input passes upward.

### **5. Mention some applications of UJT**

1. used in triggering of another device such as SCR.
2. AS a relaxation oscillator

### **6. Write the frequency equation of an Astable Multivibrator.**

The frequency equation is  $T=0.69R_1C_1$ , and  $T_2=0.69R_2C_2$

While  $T=T_1+T_2$

$F=1/T=1/0.69C(R_1C_1+R_2C_2)$

### **7. What is Schmitt trigger?**

A Schmitt trigger is a threshold circuit which uses positive feedback with loop gain greater than unity.

### **8. What is a Multivibrator?**

A multivibrator is an electronic circuit using two amplifying transistor stages each with its output connected to the input of the other by resistors and capacitors.

### **9. What is clipper?**

The circuit which is used to clip off unwanted Portion of the waveform without distorting the remaining Part of the waveform is called clipper circuit.

### **10. Under what condition would a Schmitt trigger operate as an amplifier?**

The resistance  $R_{c1}$  must be enough smaller than  $R_{c2}$  So that regeneration cannot take place and Schmitt Trigger operates as an amplifier.

## UNIT-V

### FEEDBACK AMPLIFIERS AND OSCILLATORS

1. Explain the voltage series-shunt feedback amplifier with an eq. circuit diagram

Series-shunt feedback is connected with i/p as feedback is taken from o/p.

$$V_f = \beta V_o \quad A_i = \frac{V_o}{V_i} = \text{gain of amplifier without feedback.}$$

$$V_o = V_i A \quad V_s = V_i + V_f \quad A_{vf} = \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$$

Input impedance: voltage dependent voltage source.

$$V_i = V_s - V_f = R_i I_i \quad Z_{if} = \frac{V_i}{I_i} = Z_i (1 + \beta A)$$

Output impedance:  $V_o = I Z_o + A V_i$

$$V_o (1 + \beta A) = I Z_o \quad Z_{of} = \frac{V_o}{I_o} = \frac{Z_o}{1 + \beta A}$$

- 2) Explain the current shunt-series feedback amplifier with eq.

Block diagram output current is taken as feedback parameter and is fed in parallel with input circuit.

Current gain  $I_o/I_i$  feedback factor  $\beta = I_f/I_o$

$$A_f = \frac{A}{1 + \beta A}$$

Input impedance:  $I_s = \frac{V_i}{R_i} (1 + \beta A)$ ;  $R_{if} = \frac{V_i}{I_s} = \frac{R_i}{1 + \beta A}$

output impedance:  $I_o = \frac{V_o}{R_o} - \beta I_o$   $R_{of} = \frac{V_o}{I_o} = R_o (1 + \beta A)$

Gain  $\downarrow$ , Stability  $\uparrow$ , NOISE  $\downarrow$ , Distortion  $\downarrow$

3. Describe the characteristics of Negative feedback.

When the feedback is in opposition to the i/p, the i/p signal reduced. - Negative feedback.  $V_i = V_s - V_f$

$$i_i = i_s - i_f$$

- \* Reduces the gain of the amplifier
- \* Reduces the noise, distortion & instability
- \* Increases bandwidth.
- \* Used in Amplifiers.

$$A_f = \frac{V_o}{V_s} = \frac{V_o}{V_i + V_f}$$

$$A_f = \frac{A}{1 + A\beta}$$

$|A_f| < |A|$ , gain decreases.

4. Describe the characteristics of positive feedback.

When the feedback is in phase to the input, the i/p signal increases. - positive feedback / regenerative / direct.

$$\rightarrow V_i = V_s + V_f \quad ; \quad \rightarrow i_i = i_s + i_f$$

- \* increases the gain, noise, distortion,
- \* reduces the stability of an amplifier.
- \* Used in oscillators.

$$V_f = \beta V_o$$

$$A_f = \frac{V_o}{V_s} = \frac{V_o}{V_i - V_f}$$

$$A_f = \frac{A}{1 - A\beta}$$

$|A_f| > |A|$  - gain increases.

5) Comparison of positive & Negative feedback.

- |              |                                       |
|--------------|---------------------------------------|
| * Gain       | * Stability                           |
| * Noise      | * Input and output resistance changes |
| * Distortion | * Application.                        |
| * Bandwidth  |                                       |

6) Explain the principle of operation and derive the expression for Wein bridge oscillator.

Wein bridge Oscillator - low frequencies in the range of kHz to 1 MHz.

✓ Block diagram

✓ Equivalent circuit

\* Used in audio generator.

\* Consists of two stage RC coupled amplifier

\* O/p of amplifier  $\rightarrow$  i/p of bridge.

\* O/p vge & i/p voltage = 0

\* Not produce any phase shift.

\* Continuous undamped oscillations are produced.

$\Rightarrow$  Which uses both positive & negative feedback.

$$\frac{R_1}{R_2} = 2 + j \left( \frac{R_2 X_C^2}{R_1 X_C} \right) \Rightarrow \frac{R_1}{R_2} = 2$$

$$\Rightarrow f = \frac{1}{2\pi RC} \Rightarrow V_1 = V_2 = \frac{1}{3} V_o \Rightarrow |A_v| \geq 3$$

7) Explain the principle of operation and derive the expression for Colpitts oscillator.

Colpitts Oscillator - Emitter tap is connected b/w  $C_1$  &  $C_2$ .

✓ Block diagram

✓ Equivalent ckt

\* Uses tapped capacitance

\* O/p is taken out of the inductor by transformer coupling.

\*  $C_b$  conveys feedback from c to B cat.

\*  $C_1, C_2$  acts as alternating voltage divider.

$$* Z_1 = \frac{-j}{\omega C_1} \quad Z_2 = \frac{-j}{\omega C_2} \quad Z_3 = j\omega L$$

$$\Rightarrow f = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}$$

$$\Rightarrow -h_{fe} = \frac{C_2}{C_1} \Rightarrow \text{the condition for maintenance of oscillations}$$

8) Derive the expression and characteristics of RC phase shift oscillator

RC phase shift oscillator - Using BJT.

- Positive feedback required
- frequency determining network introduce phase shift of  $180^\circ$ .
- Obtain by 3 section - Each  $60^\circ$
- Continuous damped oscillation produced.

$\Rightarrow \frac{1}{h_{oe}} \gg R_L$ , effect neglected  $\Rightarrow h_{ie} \ll 1$ ,  $h_{ie} V_2$  - neglected.

$$\begin{vmatrix} R+R_L-jX_C & -R & h_{fe}R_L \\ -R & 2R-jX_C & -R \\ 0 & -R & 2R-jX_C \end{vmatrix} = 0 \Rightarrow f = \frac{1}{2\pi RC \sqrt{6 + \frac{4R_L}{R}}}$$

$\Rightarrow h_{fe} = 23 + 29 \frac{R}{R_L} + \frac{4R_L}{R} \Rightarrow$  condition for sustained oscillation.

$$\Rightarrow f = \frac{1}{2\pi \sqrt{6} RC}$$

9) Derive the expression and characteristics of Hartley oscillator.

Hartley oscillator - Resistor & capacitor  $C_5$  provide stabilized voltage divider bias.

- FDM - C AL. → feedback b/w i/p & o/p thro transformer action.
- Equivalent circuit
- Block diagram
- RFC provides DC load for collector.
- $C_5$  blocks DC. → D.C at zero frequency.
- FET → amplifying device.
- $Z_1 = j\omega L_1 + j\omega M$   $Z_2 = j\omega L_2 + j\omega M$   $Z_3 = -j/\omega C$

$$\Rightarrow f = \frac{1}{2\pi \sqrt{(L_1 + L_2 + 2M) C}} \Rightarrow h_{fe} = \frac{L_1 + M}{L_2 + M}$$

10) Explain the operation and advantages of crystal oscillator.

Crystal oscillator - frequency of LC depends on value of tank ckt.

- \* Values change with time, temperature etc.,
- \* piezo-electric crystal is used.
- \* Quartz, tourmaline, Rochelle salt.
- \* series LCR ckt shunted by  $C_m$ .

$$\Rightarrow f_s = \frac{1}{2\pi\sqrt{LC}} \quad * \text{ parallel resonance, } f_p = \frac{1}{2\pi\sqrt{L C_T}}$$

$$\Rightarrow C_T = \frac{C C_m}{C + C_m}$$

- \* positive feedback provided by capacitive voltage divider  $\frac{C_2}{C_1 + C_2}$ .
- \* CE produces  $180^\circ$  phase shift.

Advantages :-

- \* High frequency stability
- \* High Q-factor.
- \* Low cost
- \* Simple construction
- \* highest oscillating frequencies.