

Question Paper Code: 53116

B.E./B.Tech. Degree Examination, November/December 2010

Third Semester

Electronics and Communication Engineering

EC 2205 – ELECTRONIC DEVICES AND CIRCUITS – I

(Regulation 2008)

Time:

(Regulation)

Maximum: 100 Marks

Three Hours

Questions

(Regulation 2008)

1. How can collector current be stabilized with respect to I_{CO} variations?
2. Derive for the stability factor S for a Fixed Bias circuit.
3. Define CMRR.
4. Draw a Darlington amplifier with Bootstrapp arrangement.
5. Why common base amplifier is preferred for high frequency signal when compared to common emitter amplifier?
6. Calculate the cut-off frequency due to C_1 and C_2 in the circuit shown in figure 1.

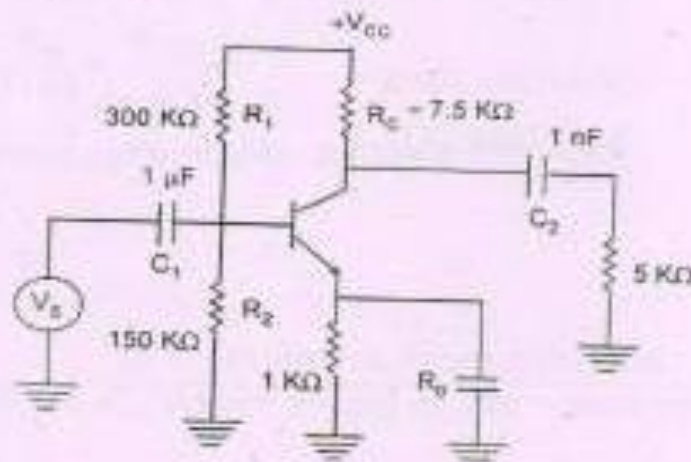


Fig. 1

7. What is meant by cross over distortion in class B power amplifier and how it is corrected?

8. A BJT has a maximum power dissipation of 2W at ambient temperature of 25°C and maximum junction temperature of 150°C , find its thermal resistance.
9. Briefly explain the working of Zener regulator.
10. Derive the ripple factor of induction filter connected to FWR.

PART B—(5 × 16 = 80 Marks)

11. (a) Draw a Self (voltage divider) Bias and derive all the stability factors S , S' and S'' . (16)
- (or)
11. (b) (i) Locate the operating point of the circuit shown. (Figure 1). (8)

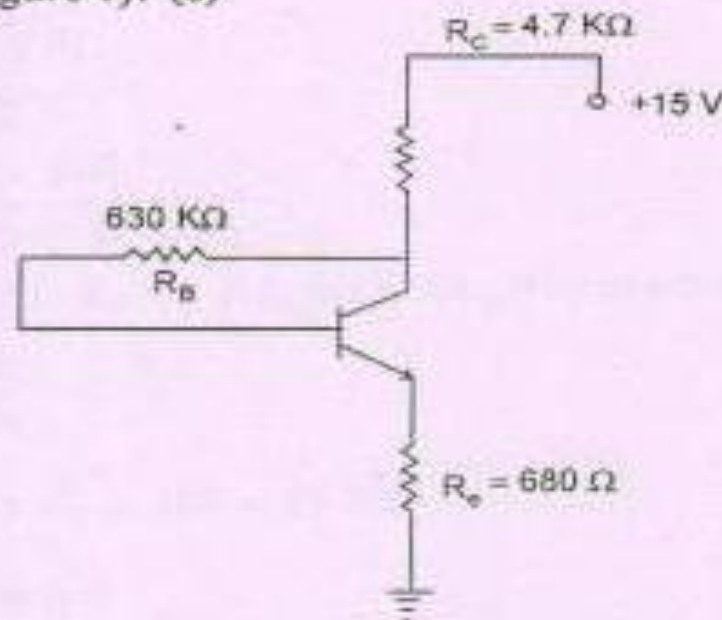


Fig. 1

$$V_{ce} = 15V$$

$$h_{fe} = 200.$$